


107 學年度四技二專第二次聯合模擬考試 電機與電子群 專業科目(一) 詳解

107-2-03-4、107-2-04-4

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25
D	C	A	C	D	A	C	D	D	A	B	D	C	A	C	D	B	A	B	B	B	D	D	D	A
26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47	48	49	50
A	C	B	A	D	A	A	C	C	B	C	D	C	B	D	C	A	C	B	B	B	B	D	C	A

第一部分：電子學

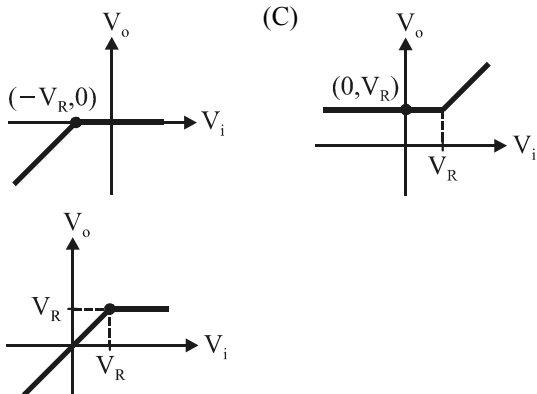1. (A) FET 為主要元件
(B) 4C 為元件、通訊、計算、控制
(C) 屬 ULSI，零件數 100000 個以上
2. (A) 導體沒有擴散電流
(B) 均隨溫度上升，電阻值下降
(D) 不帶電
3. (A) 漏電流不隨逆偏大小改變
4. (C) 穩定度不佳
5. BE 接面順偏，BC 接面逆偏
6. (B)




7. $I_B = \frac{I_E}{1+\beta} = \frac{1\text{ m}}{100} = 0.01\text{ mA}$
 $V_E = I_E \cdot R_E = V_{CC} - I_C R_C - V_{CE} = 12 - 4 - 5 = 3\text{ V}$
 $R_B = \frac{V_{CC} - V_{BE} - V_E}{I_B} = \frac{12 - 0.7 - 3}{0.01\text{ m}} = 830\text{ k}\Omega$

9. (A) 通道長度調變
(B) $\alpha = \frac{I_C}{I_E}$ ， $I_E \uparrow$ ， $\alpha \downarrow$
(C) 共集極輸出阻抗最低

10. $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$ ， $1\text{ m} = 4\text{ m} \left(1 - \frac{V_{GS}}{-2}\right)^2$
 $V_{GS} = -1, -3$ (不合)， $V_{GS} = -1 = V_G - V_S = 5 - V_S$
 $V_S = 6\text{ V}$ ， $R_S = \frac{6}{I_D} = 6\text{ k}\Omega$
 $V_{DD} = I_D \times R_D + V_{DS} + I_D R_S \Rightarrow R_D = 4\text{ k}\Omega$

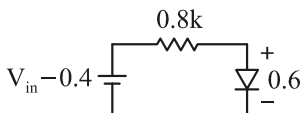11. $R_{th} = 4\text{ k} // 1\text{ k} = 0.8\text{ k}$ ， $E_{th} = V_{in} - 0.4$



$\Rightarrow V_{in} = 1$ 時導通， $I_D = \frac{V_{in} - 1}{0.8\text{ k}} = (1.25V_{in} - 1.25)\text{ mA}$

12. (A) $V_Z < 6\text{ V}$ ，稽納崩潰
(B) $P_{Z(max)} = 30\text{ m} \times 5 = 150\text{ mW}$
(C) $10 \times \frac{500}{R+500} \geq 5\text{ V}$ ， $R \leq 500\text{ }\Omega$ ， $R_{max} = 500\text{ }\Omega$
(D) $R_{min} = \frac{(10 - V_Z)}{I_{ZM} + I_L} = \frac{10 - 5}{30\text{ m} + 10\text{ m}} = 125\text{ }\Omega$


13. (A) PIV 值 = 20 V

(B) $C \cdot V_{r(p-p)} = \frac{20}{10\text{ k}} \times \frac{1}{100}$ ， $V_{r(p-p)} = \frac{1}{50\text{ k} \cdot C}$

$V_{r(rms)} = \frac{1}{100\sqrt{3} \cdot k \cdot C}$ ， $r\% \approx \frac{100\sqrt{3} \times 10^3\text{ C}}{20} < 1.2\%$
 $C > 24\text{ }\mu\text{F}$

(C) $C \cdot V_{r(p-p)} = \frac{20}{10\text{ k}} \times \frac{1}{100}$ ， $V_{r(p-p)} = \frac{1}{50\text{ k} \cdot C} < 0.1$
 $C > 200\text{ }\mu\text{F}$

- (D) 沒變

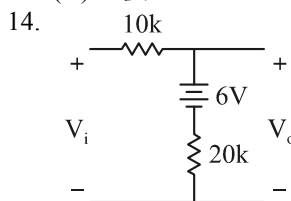


$V_i = 15\text{ V}$ 時， $\frac{V_o - 15}{10\text{ k}} + \frac{V_o - 6}{20\text{ k}} = 0$ ， $V_o = 12\text{ V}$

$V_i = 3\text{ V}$ 時， $V_o = 3\text{ V}$ ， $x + y = 15$

15. $\frac{V_o}{V_i} = \frac{-g_m V_{gs} (R_D // R_L)}{V_{gs}} = -0.5\text{ m} \times 5\text{ k} = -2.5$

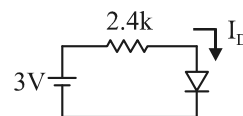16. 以二極體兩端取載維寧
 $E_{th} = 3\text{ V}$ ， $R_{th} = 2.4\text{ k}$

$I_D = \frac{3}{2.4\text{ k}} = \frac{5}{4}\text{ mA}$



$I_1 = I_4 = \frac{7.5}{3\text{ k}} = 2.5\text{ mA}$ ， $I_2 = I_3 = \frac{7.5}{2\text{ k}} = 3.75\text{ mA}$

17. (A) 只有 D 是增強型
(C) B 為空乏型 P 通道 FET
(D) C 為空乏型 N 通道 FET

18. $Z_i = R_s // \frac{1}{g_m} = 2 \text{ k} // 250 \approx 220 \Omega$

19. $Z_{ib} = (4 \text{ k} // 12 \text{ k}) \times 50 \times 80 = 12 \text{ M}\Omega$

$\frac{i_o}{i_i} = \frac{1}{4} \times 80 \times 50 \times \frac{3}{4} = 750$

20. 等效電路如右圖所示

$$V_{BB} = \frac{\frac{+6}{R_1} + \frac{-6}{R_2} + \frac{-6}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$\Rightarrow V_{BB} = -4 \text{ V}$

$\because \beta \text{ 極大}, \therefore I_B \approx 0 \text{ A} \Rightarrow V_{BB} = V_B = -4 \text{ V}$

$V_E = -3.3 \text{ V}, I_E = \frac{5.7 - (-3.3)}{3 \text{ k}} = 3 \text{ mA}$

$\because I_B \approx 0 \text{ A}, \therefore I_C = I_E$

$V_C = -12 + 3 \text{ mA} \times 2 \text{ k} = -6 \text{ V}$

$V_{EC} = -3.3 - (-6) = 2.7$

21. $40 \text{ dBm} = 10 \log \frac{P_o}{1 \text{ mW}}, P_o = 10 \text{ W} = \frac{V_3^2}{250}, V_3 = 50 \text{ V}$

$V_1 = A_{v1} \cdot V_i = 50 \cdot 50 \mu = 2.5 \text{ mV}$

$A_{v2} = 26 \text{ dB} = 20 \log \frac{V_2}{V_1}$

$\log \frac{V_2}{V_1} = 1.3 = \log 20, \frac{V_2}{V_1} = 20$

$V_2 = 2.5 \text{ mV} \times 20 = 50 \text{ mV}, A_{v3} = \frac{50}{50 \text{ m}} = 1000$

$A_{vT} = 20 \log \frac{50}{50 \mu} = 120 \text{ dB}$

22. $I_B = \frac{3 - 0.7}{5 \text{ k} + 100 \text{ k}} = \frac{2.3}{105 \text{ k}} \approx 22 \mu$

$I_{C(sat)} = \frac{6 - 0.2}{2.9 \text{ k}} = 2 \text{ mA}, \beta I_B > I_{C(sat)} \Rightarrow \text{飽和}$

$3 = I_B \times 5 \text{ k} + 0.7 + (I_B + I_C) \times 1 \text{ k} \Rightarrow I_B = 53 \mu\text{A}$

$6 = I_C \times 1.9 \text{ k} + 0.2 + (I_B + I_C) \times 1 \text{ k}$

23. $Z_i = 9 \text{ k} + [950 \text{ k} // (1 \text{ k} + 100 \times 0.3 \text{ k})]$
 $\approx 9 \text{ k} + 30 \text{ k} = 39 \text{ k}$


$Z_o = 300 // \frac{1 \text{ k} + 950 \text{ k} // 9 \text{ k}}{100} \approx 300 // 100 = 75 \Omega$

24. (A) 閘極須為高摻雜

(B) $V_{GD} \geq V_p$

(C) MOSFET 製程簡單

25.

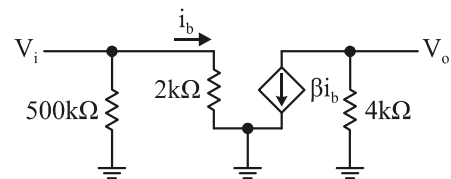

$A_v = \frac{V_o}{V_i} = \frac{-\beta i_b \cdot 4 \text{ k}}{i_b \cdot 2 \text{ k}} = -198$

第二部分：基本電學

26. (B) 中子質量最大

(C) 形成正離子

(D) 不一定相等

27. (C) 繞線型可承受之功率較大

28. $R_{AB} = [4 // 6 + 2 // 8] // 4 = 2 \Omega$

29. $I_2^2 \times 8 = 18, I_2 = 1.5 \text{ A}$


$V = 1.5 \times 25 = 37.5 \text{ V}$

$I_1 = \frac{V}{5} = 7.5 \text{ A}$


$I = I_1 + I_2 = 9$

$E = 2.5 \times 9 + 37.5 = 60$


$P_T = 9 \times 60 = 540 \text{ W}$

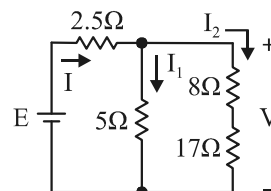

30.

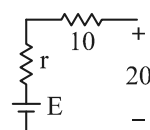

$E = 20 \text{ V}$

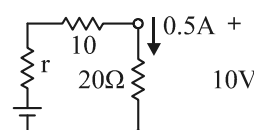

$r = \frac{20 - 10 - 5}{0.5} = 10 \Omega$

31. $7I_1 - 4I_2 - 3I_3 = 18$

$-4I_1 + 11I_2 - I_3 = 2$

$-3I_1 - I_2 + 7I_3 = -5$

$\Rightarrow a_{12} + a_{23} + a_{33} = -4 - 1 + 7 = 2$

33. (C) 正電荷可單獨存在

34. RL 串: $\tau = \frac{2 \text{ m}}{10} = 0.2 \text{ ms} = \text{A}$

RC 並: $\tau = 100 \text{ k} \cdot 0.01 \mu = 1 \text{ ms}, B = 5\tau = 5 \text{ ms}$

$5A + B = 1 \text{ ms} + 5 \text{ ms} = 6 \text{ ms} = 0.006 \text{ s}$


35. $\frac{I'}{I} = \frac{4.5}{18} = \frac{1}{4} \Rightarrow \frac{R'}{R} = \frac{I}{I'} = 4, R' = 4R, \text{電阻} = \rho \cdot \frac{\ell}{A}$

$\because \text{體積不變}, \ell \text{ 變 } k \text{ 倍} \Rightarrow A \text{ 變 } \frac{1}{k} \text{ 倍} \Rightarrow \text{電阻變 } k^2 \text{ 倍}$

$\therefore k = 2, \ell' = 2\ell = 40 \text{ cm} \Rightarrow \text{需拉長 } 20 \text{ cm}$

36. $I_{6\Omega} = \frac{24}{6} = 4 \text{ A}$


37. S 按下瞬間，電容短路，電感開路

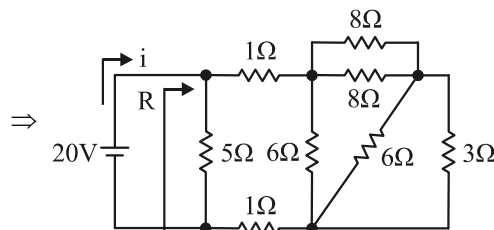

$$R = \{[(3//6+8//8)//6]+1+1\} // 5 = 5 // 5 = 2.5 \Omega$$


$$i = \frac{20}{2.5} = 8 \text{ A}$$

38. 中垂線定理

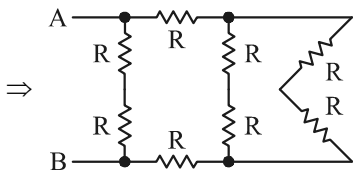

$$R_{AB} = [(2R // 2R) + 2R] // 2R = 3R // 2R = 18 // 12 = 7.2 \Omega$$

39. 壓流互換

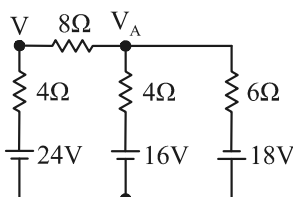


密爾門：

$$V_A = (12 // 4 // 6) \times \left(\frac{24}{12} + \frac{16}{4} + \frac{-18}{6} \right) = 6 \text{ V}$$

$$V = 24 - \frac{24-6}{12} \times 4 = 18 \text{ V}$$

40.

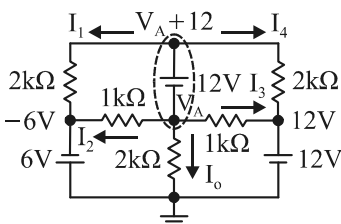

$$I_1 + I_2 + I_0 + I_3 + I_4 = 0$$

$$\frac{V_A + 12 + 6}{2 \text{ k}} + \frac{V_A + 6}{1 \text{ k}} + \frac{V_A}{2 \text{ k}} + \frac{V_A - 12}{1 \text{ k}} + \frac{V_A + 12 - 12}{2 \text{ k}} = 0$$

$$7V_A = -6, \quad V_A = -\frac{6}{7}, \quad I_0 = \frac{-6}{2 \text{ k}} = -\frac{3}{7} \text{ mA}$$

41. $\alpha_{20} = \frac{1}{|T_0| + 20} = \frac{1}{222}, \quad |T_0| = 202$

$$\frac{150}{10} = \frac{T + 202}{28 + 202}, \quad T + 202 = 3450, \quad T = 3248^\circ \text{C}$$

42. $C_T = (10 \mu + 20 \mu) // 10 \mu // 5 \mu = \frac{30}{1+3+6} \mu = 3 \mu \text{F}$

43. 電源切斷 Q 不變

$$C = \epsilon \frac{A}{d}, \quad W = \frac{1}{2} CV^2 = \frac{1}{2} QV = \frac{1}{2} \frac{Q^2}{C}$$

$$d' = \frac{1}{2} d \Rightarrow C' = 2C \Rightarrow W' = \frac{1}{2} W = \frac{1}{2} \times 8 = 4 \text{ J}$$


44. 電感為串聯互消

$$M = k\sqrt{L_1 L_2} = 1 \text{ mH}$$

$$L_T = L_1 + L_2 - 2M = 11 \text{ mH}, \quad A = 11$$


$$W = \frac{1}{2} L_1 I^2 + \frac{1}{2} L_2 I^2 - M I^2 = 18 + 8 - 4 = 22 \text{ mJ}, \quad B = 22$$

45. 等效：

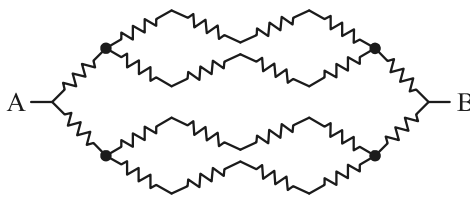

$$R_{AB} = [(4R // 4R) + 2R] // [(4R // 4R) + 2R] = 4R // 4R = 2R = 20 \Omega$$

46. ABC 作 Δ-Y 轉換

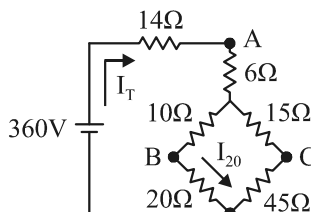

$$R_T = (30 // 60) + 6 + 14 = 40$$

$$I_T = \frac{360}{40} = 9, \quad I_{20} = 9 \times \frac{60}{60+30} = 6 \text{ A}$$


$$V_A = 360 - 9 \times 14 = 234 \text{ V}$$

$$V_B = 20 \times 6 = 120 \text{ V}$$

$$I = \frac{234 - 120}{20} = 5.7 \text{ A}$$

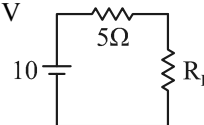47. $R_{th} = 2 + 3 = 5 \Omega, \quad E_{th} = 6 + 4 = 10 \text{ V}$

$$R_L = 5 \Omega \text{ 時}, \quad P_{max} = \frac{5^2}{5} = 5 \text{ W}$$



48. (A) $R = \frac{\ell}{\mu A} = \frac{2\pi \times 10^{-2}}{4\pi \times 10^{-7} \times 10^3 \times 2 \times 10^{-4}} = \frac{1}{4 \times 10^{-6}} = 2.5 \times 10^5 \text{ AT/Wb}$

(B) $\phi = \frac{N_1 I_1}{R} = \frac{100 \times 20}{2.5 \times 10^5} = 8 \times 10^{-3} \text{ Wb}$

$$B = \frac{\phi}{A} = \frac{8 \times 10^{-3}}{2 \times 10^{-4}} = 4 \times 10 \text{ Wb/m}^2 = 4 \times 10^5 \text{ Gauss}$$


(C) $L_1 = \frac{N_1 \phi_1}{I_1} = \frac{100 \times 8 \times 10^{-3}}{20} = 40 \text{ mH}$

(D) $M = \frac{N_2 \phi_{12}}{I_1} = \frac{50 \times 8 \times 10^{-3}}{20} = 20 \text{ mH}$

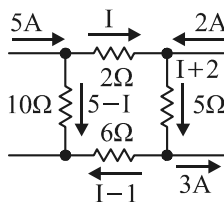49. 由 KVL 知

$$2I + 5(I+2) + 6(I-1) = 10(5-I)$$

$$23I = 46, \quad I = 2 \text{ A}, \quad \text{故選(C)}$$



$$50. E_{th} = 24 \text{ V}, R_{th} = 8 \Omega, \tau = \frac{2}{8} = \frac{1}{4}$$

$$i_L(t) = 3 + (0 - 3)e^{-\frac{t}{4}} = 3(1 - e^{-4t})$$

$$V_L(t) = 24 - 24(1 - e^{-4t}) = 24e^{-4t}$$

$$V_{4\Omega} = 4 \times 3(1 - e^{-4t}) = 12(1 - e^{-4t})$$

$$V_R(t) = V_{4\Omega} + V_L(t) = 12 - 12e^{-4t} + 24e^{-4t} = 12 + 12e^{-4t}$$

