

109 學年度四技二專第一次聯合模擬考試 電機與電子群 專業科目(一) 詳解

109-1-03-4、109-1-04-4

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25
C	B	C	B	D	A	B	D	D	C	C	A	D	A	D	B	C	A	B	D	D	C	A	B	A
26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47	48	49	50
D	A	B	B	C	A	C	A	D	A	D	C	B	B	A	B	B	D	B	C	C	D	C	A	A

第一部分：電子學


1. $I_B = \frac{9.7 - 0.7}{200\text{ k} + (1 + 99) \times 1\text{ k}} = \frac{9}{300\text{ k}} = 0.03\text{ mA}$

$I_C = \beta I_B = 99 \times 0.03\text{ mA} = 2.97\text{ mA}$

$I_{C(\text{sat})} = \frac{9.7}{1\text{ k} + 1\text{ k}} = 4.85\text{ mA} > I_C$

$\therefore V_o = 9.7 - 2.97\text{ mA} \times 1\text{ k}\Omega = 6.73\text{ V}$

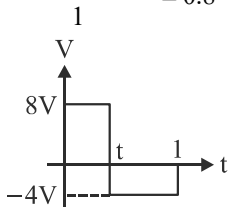2. $\frac{8t + (-4)(1-t)}{1} = 0.8, 12t = 4.8 \quad \therefore t = 0.4$



$\therefore D\% = \frac{t}{1} \times 100\% = \frac{0.4}{1} \times 100\% = 40\%$

3. 當降低基極寬度或提高射極摻雜濃度時，則 $I_C \uparrow$ 、 $I_B \downarrow$ 、 $\beta \uparrow$

5. $I_L = \frac{5\text{ V}}{200\ \Omega} = 25\text{ mA}$

$I_z = \frac{12\text{ V} - 5\text{ V}}{200\ \Omega} - I_L = 35\text{ mA} - 25\text{ mA} = 10\text{ mA}$

$P_z = V_z \cdot I_z = 5\text{ V} \times 10\text{ mA} = 50\text{ mW}$

6. $r = \frac{2.4}{R_L \cdot C} \Rightarrow 0.0001 = \frac{2.4}{20\text{ k}\Omega \cdot C \cdot \mu\text{F}}$

$C = \frac{2.4}{0.0001 \times 20} = 1200\ \mu\text{F}$

9. 過渡電容 $C_T = \epsilon \frac{A}{d}$ ，逆偏 \uparrow ， $d \uparrow$ ， $C_T \downarrow$

擴散電容 $C_D = \frac{\tau I_D}{\eta V_T}$ ， $I_D \uparrow$ ， $C_D \uparrow$

10. $\therefore n_i^2 = p \times n$

$\therefore (1.5 \times 10^{10})^2 = p \times (\frac{5 \times 10^{22}}{10^5})$

故 $p = 0.45 \times 10^3 / \text{cm}^3$

12. (A) 操作在作用區時，E-B 接面為順向偏壓，C-B 接面為逆向偏壓

13. $R_{BB} = 12\text{ k}\Omega // 4\text{ k}\Omega = 3\text{ k}\Omega$

$V_{BB} = -12\text{ V} \times \frac{4\text{ k}}{12\text{ k} + 4\text{ k}} = -3\text{ V}$

$I_{C(\text{sat})} = \frac{12 - 0.2}{1\text{ k}\Omega + 1\text{ k}\Omega} = 5.9\text{ mA}$

$I_B = \frac{3\text{ V} - 0.7\text{ V}}{103\text{ k}\Omega} = 22.33\ \mu\text{A}$

$I_C = \beta \times I_B \doteq 2.21\text{ mA} < 5.9\text{ mA}$

$\therefore V_{EC} = 12 - 2.21\text{ mA} (1\text{ k}\Omega + 1\text{ k}\Omega) = 7.58\text{ V}$

14. $I_B = \frac{8.7\text{ V} - 0.7\text{ V}}{40\text{ k}\Omega} = 0.2\text{ mA}$

$I_C = \beta I_B = 99 \times 0.2\text{ mA} = 19.8\text{ mA}$

$I_{C(\text{sat})} = \frac{8.7\text{ V} - 0.2\text{ V}}{800\ \Omega} = 10.625\text{ mA}$


$\therefore I_C > I_{C(\text{sat})} \quad \therefore I_C = I_{C(\text{sat})} = 10.625\text{ mA}$

15. 假設 D_1 、 D_2 皆導通，運用密爾門定理，列算式如下：

$V' = (\frac{12\text{ V}}{2\text{ k}} + \frac{0\text{ V}}{2\text{ k}} + \frac{0\text{ V}}{2\text{ k}}) \times (2\text{ k} // 2\text{ k} // 2\text{ k})$

$= 6 \times \frac{2}{3} = 4\text{ V} \quad (D_1、D_2 \text{ 導通符合})$

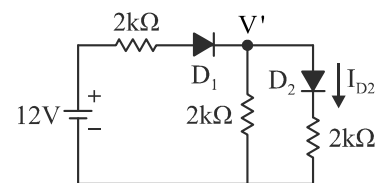$\therefore I_{D2} = \frac{V'}{2\text{ k}} = \frac{4\text{ V}}{2\text{ k}} = 2\text{ mA}$



16. $V_{p-p} = \frac{V_m \cdot t}{R_L \cdot C} = \frac{100\sqrt{2} \times \frac{1}{60}}{2\text{ k} \times 500\ \mu} = 2.36\text{ V} \doteq 2.4\text{ V}$

18. V_o 介於 $3\text{ V} \sim -7\text{ V}$ 之間，故 $V_{o(p-p)} = 10\text{ V}$

20. $\therefore I_E = \frac{8.7\text{ V} - 3\text{ V}}{1\text{ k}\Omega} = 5.7\text{ mA}$

$\therefore I_B = \frac{5.7\text{ mA}}{1 + 99} = 57\ \mu\text{A}$ ， $R_B = \frac{3 - 0.7}{57\ \mu\text{A}} \approx 40.35\text{ k}\Omega$

22. $I_{LED} = \frac{15\text{ V}}{500\ \Omega} = 30\text{ mA}$

23. 近似符合條件 $\beta \times R_C > R_B \Rightarrow R_C \uparrow R_B \downarrow$

24. $I_E = \frac{10 - 0.7}{9.3 \text{ k}\Omega} = 1 \text{ mA}$

$V_{CE} = 20 \text{ V} - 1 \text{ mA}(3 \text{ k}\Omega + 9.3 \text{ k}\Omega) = 7.7 \text{ V}$

第二部分：基本電學

27. $W = Q \times V = 3 \text{ C} \times 4 \text{ V} = 12 \text{ J}$

28. $R = \rho \times \frac{l}{A} = 2.83 \times 10^{-8} \times \frac{20 \text{ m}}{\frac{\pi}{4}(1.6 \times 10^{-3})^2} = 0.283 \Omega$

29. 黃紫黃金 = $47 \times 10^4 \pm 5\% = 446.5 \text{ k}\Omega \sim 493.5 \text{ k}\Omega$

30. $R = 51 \times 10^1 \pm 20\% = 408 \Omega \sim 612 \Omega$

$\therefore I_{\min} = \frac{24 \text{ V}}{612 \Omega} = 39.2 \text{ mA}$

31. \therefore 均勻拉長 V 不變 $l' = \frac{6}{5} V$, $A' = \frac{5}{6} A$

$R' = \rho \times \frac{l'}{A'} = \rho \times \frac{\frac{6}{5} l}{\frac{5}{6} A} = \frac{36}{25} \cdot R = \frac{36}{25} \times 50 = 72 \Omega$




32. 15°C 時 $V_{\text{THW}} = 6 \text{ V} \times \frac{2 \text{ k}}{3 \text{ k} + 2 \text{ k}} = 2.4 \text{ V}$

20°C 時 $V_{\text{THW}} = 6 \text{ V} \times \frac{1.5 \text{ k}}{3 \text{ k} + 1.5 \text{ k}} = 2 \text{ V}$

33. S ON 時, $V_{ab} = 12 \text{ V}$, S OFF 時, $V_{ab} = 0 \text{ V}$

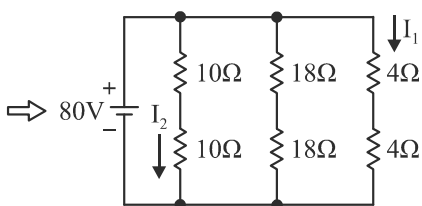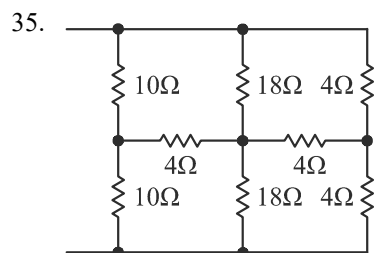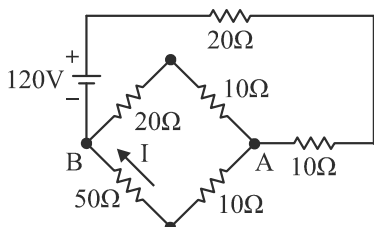34. $V_{AB} = 120 \text{ V} \times \frac{60 // 30}{20 + 10 + (60 // 30)} = 120 \times \frac{20}{50} = 48 \text{ V}$

$\therefore I = \frac{48 \text{ V}}{50 + 10} = 0.8 \text{ A}$




$I_1 = \frac{80 \text{ V}}{4 + 4} = 10 \text{ A}$, $I_2 = \frac{80 \text{ V}}{10 + 10} = 4 \text{ A}$

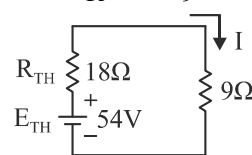36. $R_{\text{TH}} = 6 + 6 + 6 = 18 \Omega$



$E_{\text{TH}} = 4 \text{ A} \times 6 \Omega + 30 \text{ V} = 54 \text{ V}$

$\therefore P = \frac{V^2}{R} = \frac{(54 \times \frac{1}{3})^2}{9} = 36 \text{ W}$




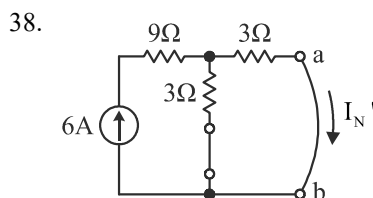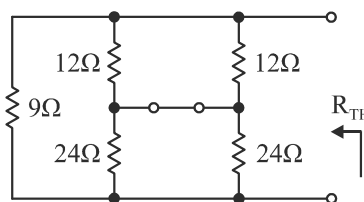37. $R_{\text{TH}} = 9 // [(12 // 12) + (24 // 24)] = 9 // 18 = 6 \Omega$

當 $R_L = R_{\text{TH}} = 6 \Omega$ 時, 可獲得最大功率



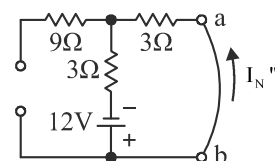$I_{N'} = 6 \text{ A} \times \frac{3 \Omega}{3 \Omega + 3 \Omega} = 3 \text{ A}$




$I_{N''} = \frac{12 \text{ V}}{3 \Omega + 3 \Omega} = 2 \text{ A}$

$\therefore I_N = I_{N'} - I_{N''} = 3 - 2 = 1 \text{ A}$


$R_N = 3 \Omega + 3 \Omega = 6 \Omega$

39. $I = \frac{12 + 12 - 6}{3 + 3 + 6} = 1.5 \text{ A}$

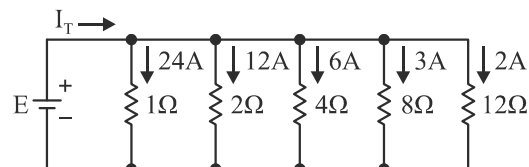40. $I_T = \frac{24 \text{ V}}{1 \Omega} + \frac{24 \text{ V}}{2 \Omega} + \frac{24 \text{ V}}{4 \Omega} + \frac{24 \text{ V}}{8 \Omega} + \frac{24 \text{ V}}{12 \Omega}$
 $= 24 \text{ A} + 12 \text{ A} + 6 \text{ A} + 3 \text{ A} + 2 \text{ A} = 47 \text{ A}$



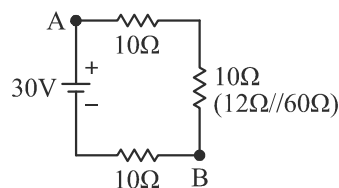
41. $V_{AB} = 30 \text{ V} \times \frac{10 \Omega + 10 \Omega}{10 \Omega + 10 \Omega + 10 \Omega} = 20 \text{ V}$



$$42. V' = \left(\frac{12\text{ V}}{3\ \Omega} + \frac{24\text{ V}}{6\ \Omega} + \frac{24\text{ V}}{6\ \Omega} \right) \times (3 // 6 // 6)\ \Omega$$

$$= 12 \times \frac{6}{4} = 18\text{ V}$$
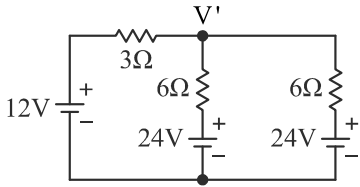
$$V_{3\ \Omega} = 18 - 12 = 6\text{ V} \quad \therefore P_{3\ \Omega} = \frac{6^2}{3\ \Omega} = 12\text{ W}$$





$$44. I_{4\ \Omega} = \frac{2\text{ A} \times 6\ \Omega}{4\ \Omega} = 3\text{ A}, \quad I_{2\ \Omega} = \frac{2\text{ A} \times 6\ \Omega}{2\ \Omega} = 6\text{ A}$$

$$\therefore I_{3\ \Omega} = 2 + 3 + 6 = 11\text{ A}$$

45. 流入 = 流出

$$3\text{ A} + 1\text{ A} + 2\text{ A} + 4\text{ A} = I_x + 4\text{ A} + 5\text{ A} + 3\text{ A}$$

$$\therefore I_x = -2\text{ A}$$

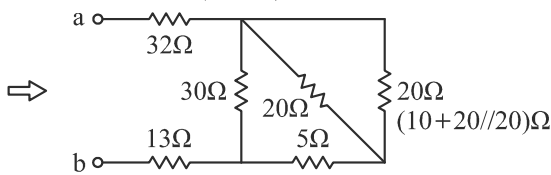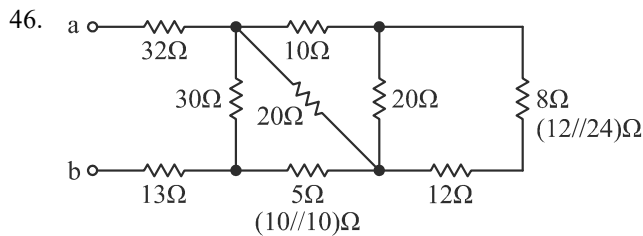

$$\therefore R_{ab} = 32 + (30 // 15) + 13 = 55\ \Omega$$

47. 藍黑橙金： $60 \times 10^3 \pm 5\%$

橙黑橙金： $30 \times 10^3 \pm 5\%$

並聯為 $20 \times 10^3 \pm 5\%$ (紅黑橙金)

48. R_1 斷路： $R_{ab} = 0\ \Omega$

$$R_2 \text{ 斷路：} R_{ab} = 15 + (30 // 15) + 10 = 35\ \Omega$$

$$R_3 \text{ 短路：} R_{ab} = 15 + (20 // 30 // 15) = 21.67\ \Omega$$

$$R_4 \text{ 短路：} R_{ab} = 15 + (20 // 10) = 21.67\ \Omega$$

$$49. V_a = 10\text{ V} \times \frac{2\ \Omega}{2\ \Omega + 3\ \Omega} - 20\text{ V} = -16\text{ V}$$

$$V_b = -50\text{ V} \times \frac{2\ \Omega}{3\ \Omega + 2\ \Omega} = -20\text{ V}$$

$$50. P_s = 30\text{ W} = \frac{E^2}{2R} \Rightarrow \frac{E^2}{R} = 60$$

$$P_p = \frac{E^2}{\frac{R}{2}} = \frac{2E^2}{R} = 2 \times 60 = 120\text{ W}$$